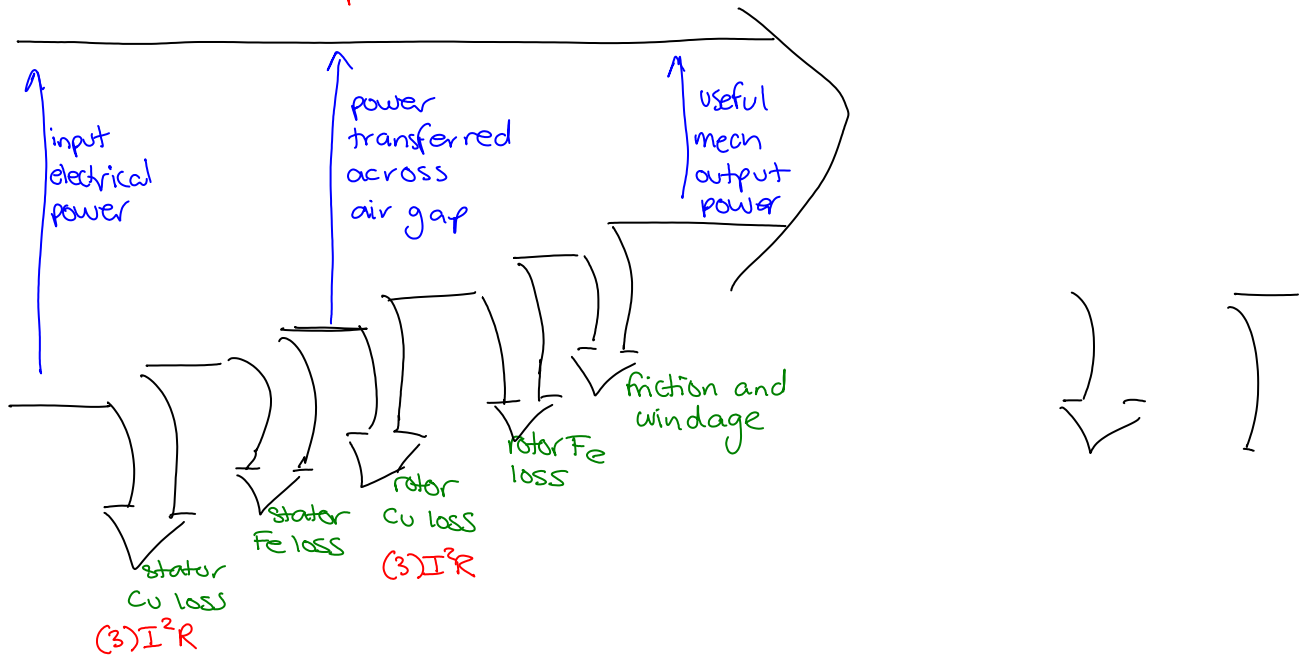



Lecture 12

Tuesday, 15 September 2009
4:36 PM

Power Balance $\frac{\text{output}}{\text{input}} = \frac{\text{input} - \text{losses}}{\text{input}} = \frac{\text{output}}{\text{output} + \text{losses}}$



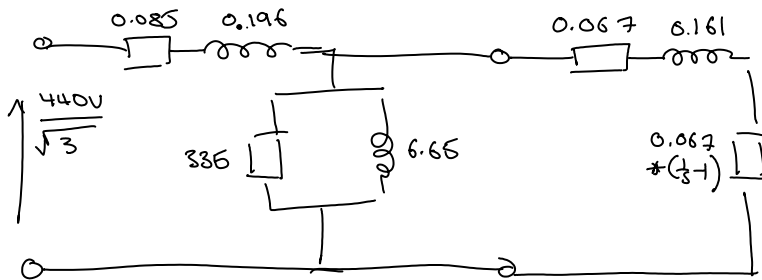
Eg: A 100hp 3 ϕ , Δ connected, 440V, 50 Hz, 8-pole induction motor has the following equivalent act parameters referred to the stator.






The total rotational & stray load losses are 2.7kw and 0.5kw respectively and may be considered constant.

Calculate for a slip of 3%

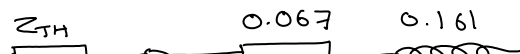- i) P_m
- ii) I_a
- iii) pf
- iv) stator active power loss
- v) N_m
- vi) η



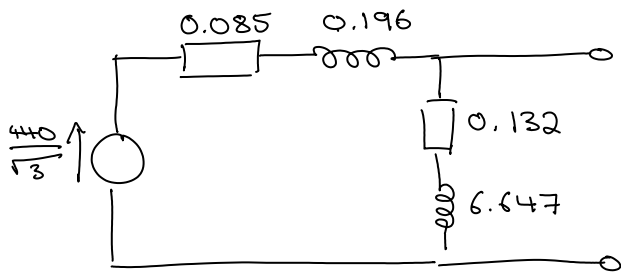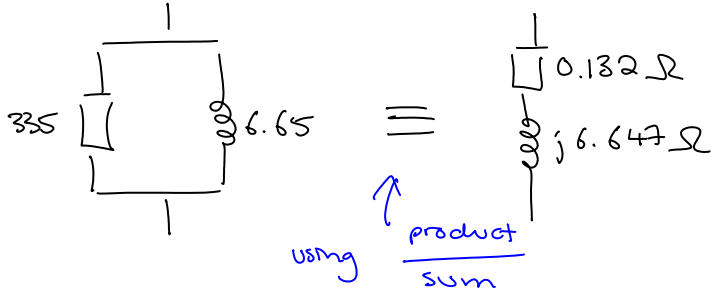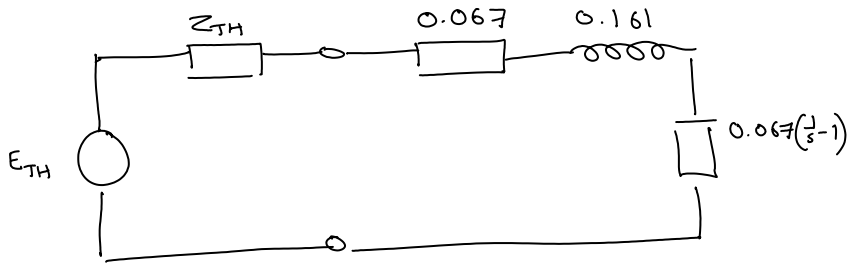

parallel


$$Z_{TH} = \frac{(0.085 + j0.196)(0.132 + j6.647)}{(0.085 + j0.196) + (0.132 + j6.647)}$$

$$= 0.0803 + j0.1913 \Omega$$

$$E_{TH} = \frac{0.132 + j6.647}{(0.132 + j6.647) + (0.085 + j0.196)} \times \frac{440}{\sqrt{3}}$$

voltage divider

$$= 246.68 \angle 0.68^\circ$$

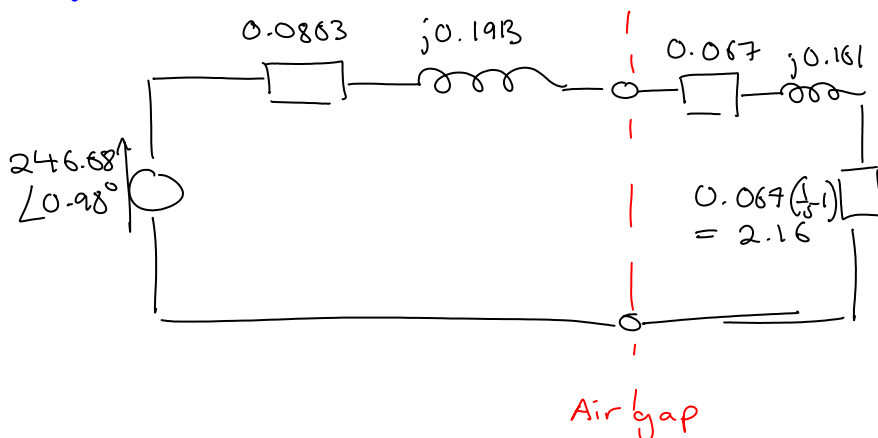

$$I_a' = \frac{E_{TH}}{(0.0803 + j0.1913) + (0.067 + j0.161) + 2.16}$$

$$= 105.4 \angle -8.0^\circ$$

$$P_{ma} = 3 I_a'^2 \left(\frac{R_r'}{s} \right)$$

$$= 3 \times (105.4)^2 \frac{0.067}{0.03}$$

$$= 74442 \text{ W}$$

$$P_m = P_{ma} (1 - s)$$

$$= 0.97 \times 74442 \text{ W}$$

$$= 72208 \text{ W}$$

$$V = I_a' \left(\frac{0.067}{s} + j0.161 \right)$$

$$= (105.4 \angle -8^\circ) \left(\frac{0.067}{0.03} + j0.161 \right)$$

$$I_{ma} = \frac{V}{0.132 + j6.647}$$

$$= 35.5 \angle -92.7^\circ$$

$$\therefore I_a = I_a' + I_{ma}$$

$$= 105.4 \angle -8^\circ + 35.5 \angle -92.7^\circ$$

$$= 114.3 \angle -26^\circ$$

$$pf = \cos \phi$$

$$= \cos 26$$

$$= 0.89 \text{ lag}$$

$$iv) \quad 3 I_a^2 \times 0.085$$

$$= 3 \times 114.3^2 \times 0.085$$

$$= 3330W$$

$$\begin{aligned} \text{Fe loss: } & 3 \frac{V^2}{K_c} \\ & = 3 \times \frac{236^2}{335} \\ & = 498W \end{aligned}$$

$$\begin{aligned} N_{ms} &= \frac{R \omega F}{P} \\ &= \frac{120 \times 50}{80} \\ &= 750 \text{ rpm} \end{aligned}$$

$$\begin{aligned} N_m &= N_{ms} (1 - s) \\ &= 727.5 \text{ rpm} \end{aligned}$$

$$\eta = \frac{P_{out}}{P_{in}}$$

$$P_m = 72208W$$

$$\begin{aligned} P_{m \text{ out}} &= 72208 - 3200 \\ &= 69008 \end{aligned}$$

$$\begin{aligned} P_{in} &= 3VI \cos \phi \\ &= 3 \times \frac{440}{\sqrt{3}} \times 114.3 \cos 26 \\ &= 78292W \end{aligned}$$

$$\eta = \frac{69008}{78292} = 88\%$$

From the equiv cct

$$I_a' = \frac{E_{TH}}{Z_{TH} + \frac{R_r'}{s} + j\omega_s L_r'}$$

$$|I_a'| = \frac{E_{TH}}{\dots}$$

$$|a| = \sqrt{\left(R_{TH} + \frac{R_r'}{s}\right)^2 + \left(X_{TH} + X_{er}'\right)^2}$$

$$\left(I_a'\right)^2 = \frac{E_{TH}^2}{\left(R_{TH} + \frac{R_r'}{s}\right)^2 + \left(X_{TH} + X_{er}'\right)^2}$$

$$\tau = \frac{P_{ma}}{\omega_{ms}}$$

$$P_{ma} = 3 I_a'^2 \frac{R_r'}{s}$$

$$\therefore \tau = \frac{3}{\omega_{ms}} \left(I_a'\right)^2 \frac{R_r'}{s}$$

$$= \frac{3}{\omega_{ms}} \left[\frac{E_{TH}^2}{\left(R_{TH} + \frac{R_r'}{s}\right)^2 + \left(X_{TH} + X_{er}'\right)^2} \right] \frac{R_r'}{s}$$

for small slip $s \rightarrow 0$

$$\left(R_{TH} + \frac{R_r'}{s}\right) \gg \left(X_{TH} + X_{er}'\right) \Rightarrow \left(R_{TH} + \frac{R_r'}{s}\right)^2 \gg \left(X_{TH} + X_{er}'\right)^2$$

and $\frac{R_r'}{s} \gg R_{TH}$

$$\begin{aligned} \therefore \tau &\approx \frac{3E_{TH}^2}{\omega_{ms}} \left(\frac{1}{\left(\frac{R_r'}{s}\right)^2} \right) \frac{R_r'}{s} \\ &= \frac{3E_{TH}^2}{\omega_{ms}} \frac{s}{R_r'} \end{aligned}$$

ie $\tau \propto s$ for a small slip.

For a large slip ($s \rightarrow 1$)

$$\left(R_{TH} + \frac{R_r'}{s}\right) \ll \left(X_{TH} + X_{er}'\right)$$

so

$$\left(R_{TH} + \frac{R_r'}{s}\right)^2 \ll \left(X_{TH} + X_{er}'\right)^2$$

$$\therefore \tau = \frac{3E_{TH}^2}{\omega_{ms}} \left[\frac{1}{\left(X_{TH} + X_{er}'\right)^2} \right] \frac{R_r'}{s}$$

ie $\tau \propto \frac{1}{s}$ for a large slip.